 


ASSIGNMENT - 2

Q.1 Design AND, OR, and NOT gate using NAND and NOR gate.


- **AND GATE USING NAND AND NOR GATE**



- **TRUTH TABLE : -**

INPUTS		OUTPUT
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1


- OR GATE USING NAND AND NOR GATE.

 

- TRUTH TABLE : -

INPUTS		OUTPUT
A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

- OR GATE USING NAND AND NOR GATE .

 


- TRUTH TABLE : -

INPUTS	OUTPUT
A	B
0	1
1	0

Q.2 Design a Half Adder and Full adder using basic gates.


- **Half Adder using Basic gates.**

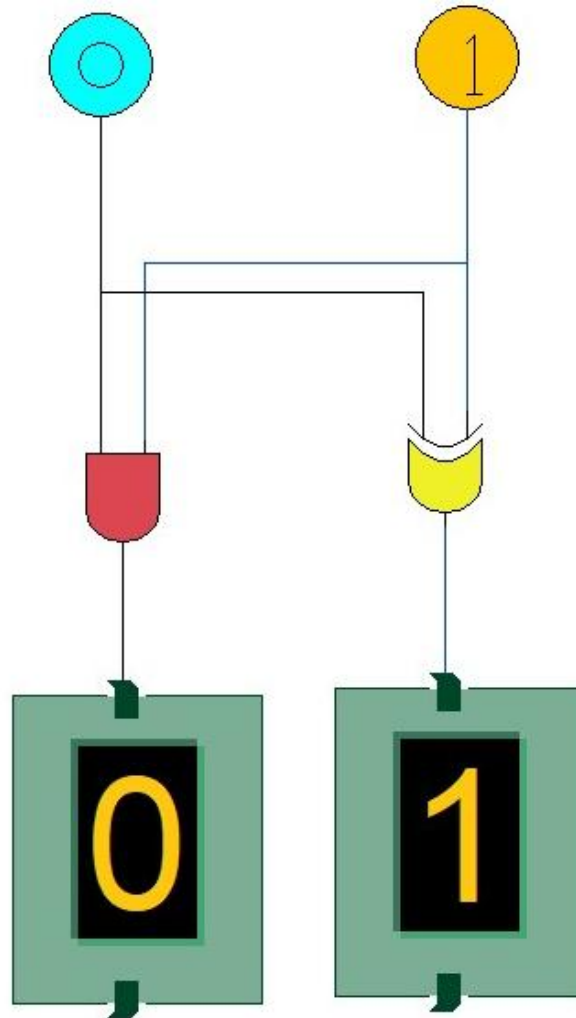

- **TRUTH TABLE : -**

INPUT		OUTPUT	
A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


- FULL ADDER USING BASIC GATES.

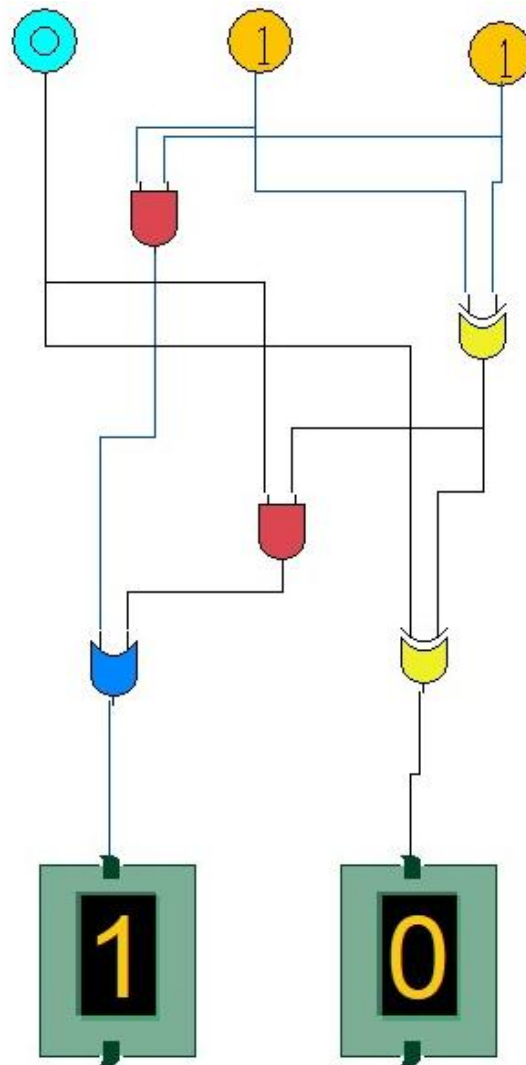

- TRUTH TABLE : -

INPUTS			OUTPUT	
A	B	Cin	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

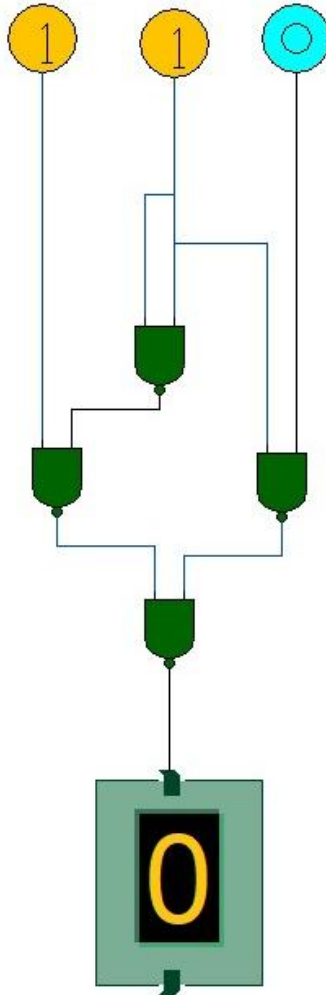
Q.3 To Design and set up 2:1 Multiplexer(MUX) using only NAND gates.



● **TRUTH TABLE : -**

SELECT LINE	INPUTS		OUTPUT
S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

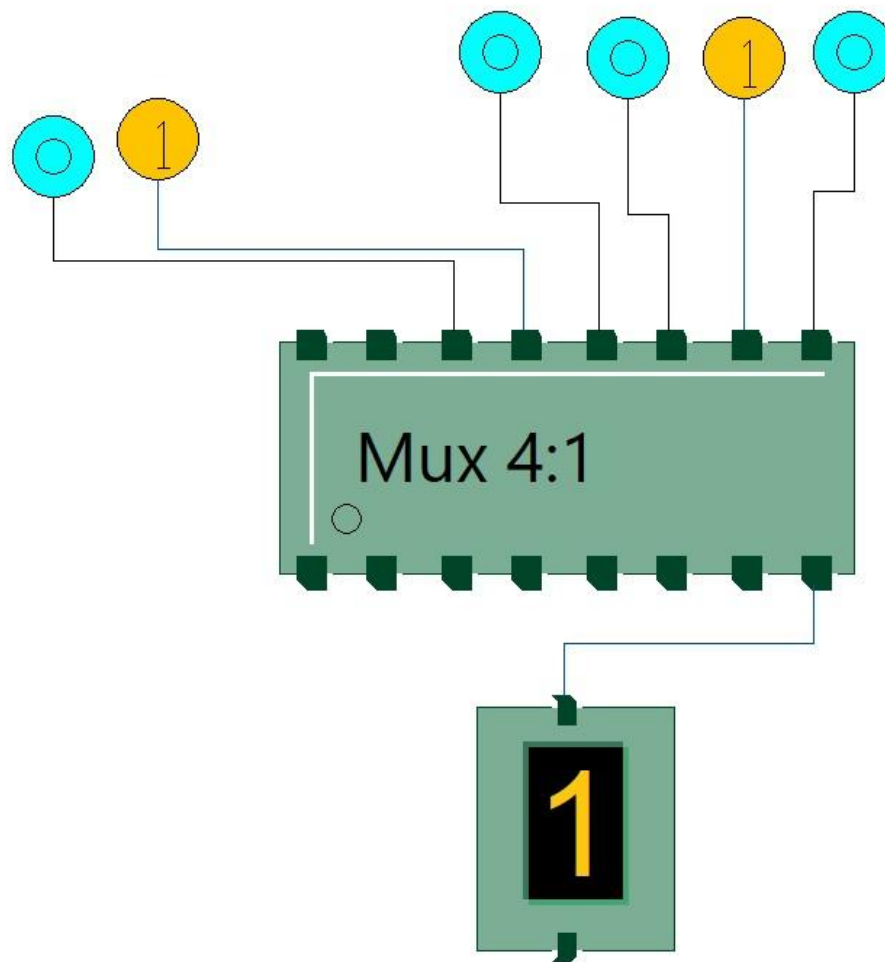
Q.4 To design and set up 4:1 Multiplexer (MUX) using in the Simulator.



● **TRUTH TABLE : -**

SELECT LINE		OUTPUT			
S1	S0	Y3	Y2	Y1	Y0
0	0	x	x	x	1
0	1	x	x	1	x
1	0	x	1	x	x
1	1	1	x	x	x

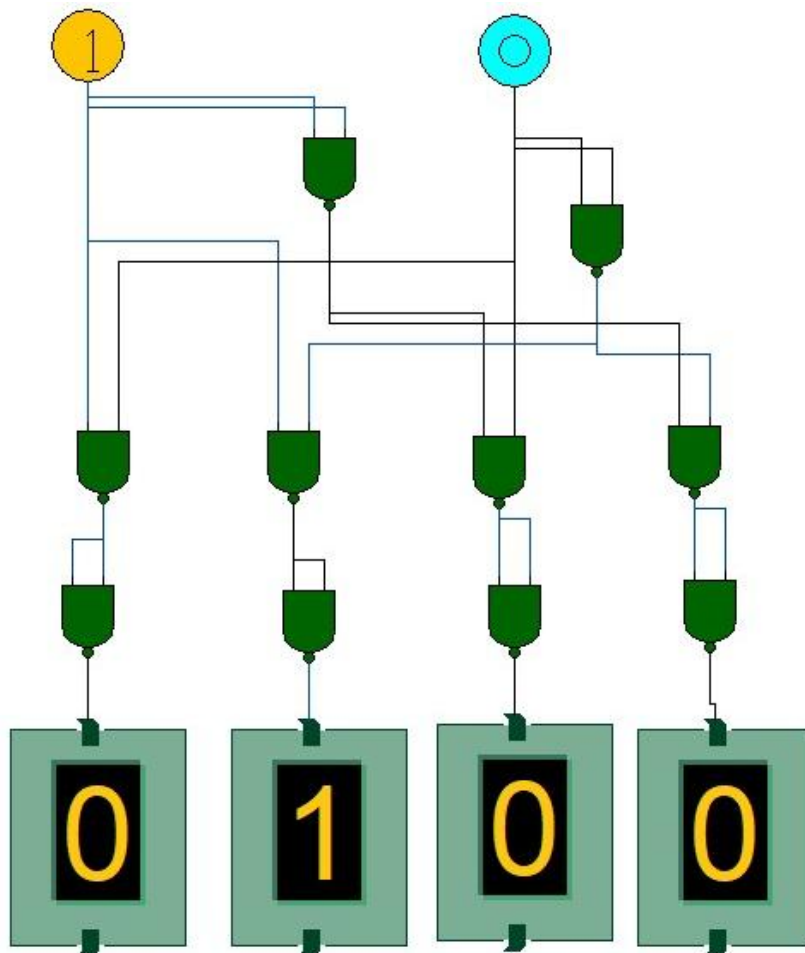
Q.5 To design and Implement 2 to 4 decoder using NAND gates.



● **TRUTH TABLE :-**

INPUTS		OUTPUT			
A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

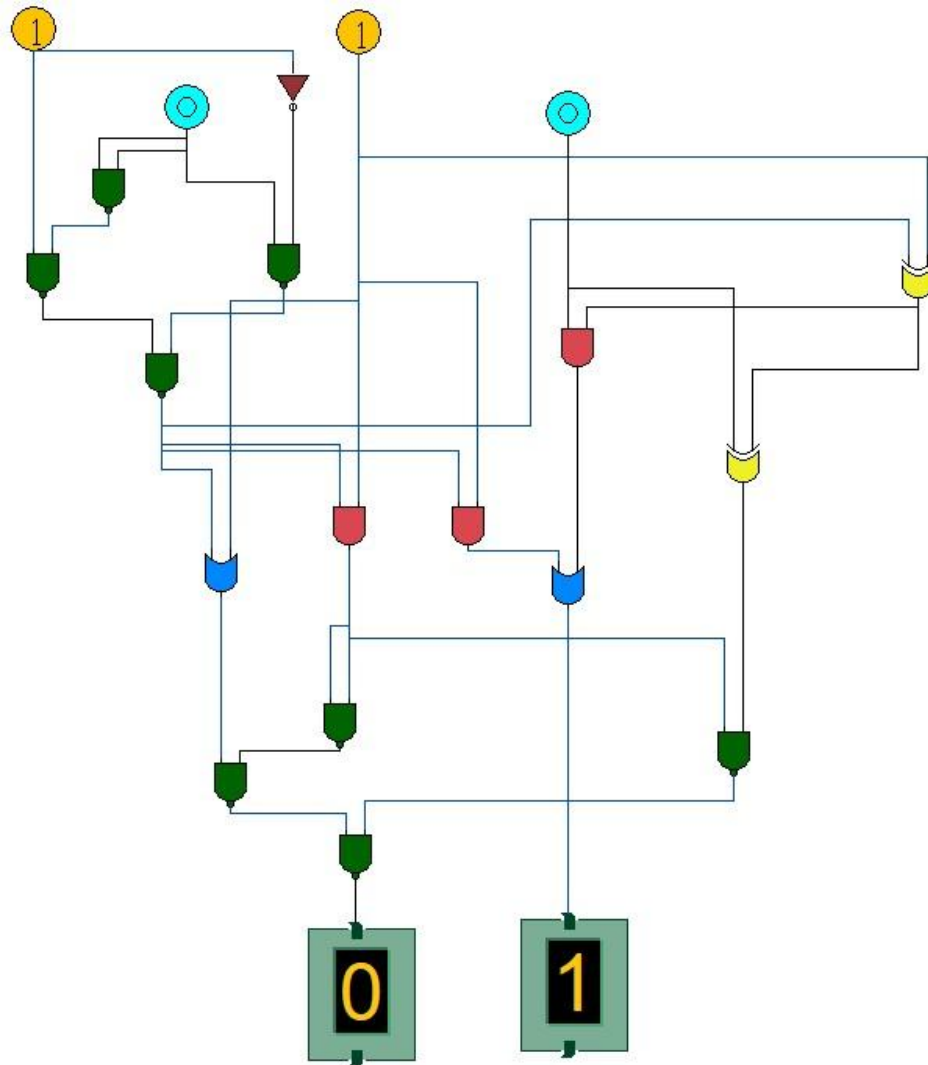Q.6 Design the Arithmetic Logical unit using basic gates.



● **TRUTH TABLE : -**

F2	F1	F0	ALU Function	Carry Out
0	0	0	A OR B	0
0	0	1	B'	0
0	1	0	AB	0
0	1	1	A+B	Carry from A+B
1	0	0	A XOR B	0
1	0	1	A XNOR B	0
1	1	0	Logic '0'	0
1	1	1	Logic '1'	0